

Solutions to Problem Set of chapter 5

Notice

Copyright of Thomas L. Floyd. Use in class only. Do not distribute unless permission is obtained from the original author.

2.


$$(b) \quad X = \overline{\overline{AB} + \overline{ACD} + \overline{DBD}}$$

4.


$$(d) \quad X = \overline{\overline{(A+B)(BC)} + D} = \overline{\overline{(A+B)(BC)}} + D = \overline{A+B} + BC + D = \overline{A} + \overline{B} + D$$

$$(e) \quad X = \overline{\overline{(AB + \overline{C})D} + \overline{E}} = \overline{\overline{(AB + \overline{C})D}} + \overline{\overline{E}} = ABD + \overline{C}D + \overline{E}$$

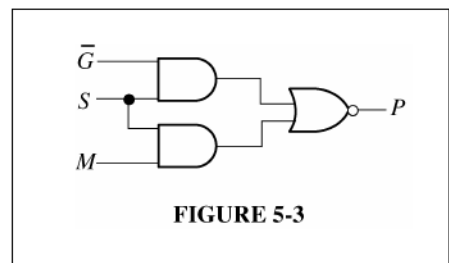8. Let G = guard, S = switch, M = motor temp, and P = power. See Figure 5-3.
 $P = \overline{\overline{GS} + MS}$




10.

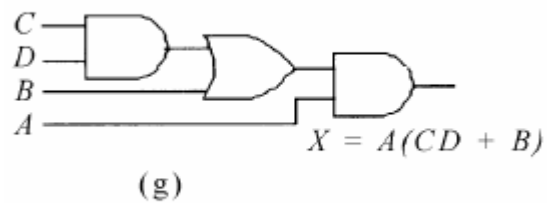

$$\begin{aligned}
 16. \quad X &= \overline{\overline{AB}(\overline{B+C})} + C = \overline{\overline{AB}(\overline{B+C})\overline{C}} = \overline{\overline{AB}(\overline{B+C})\overline{C}} = \overline{(A+B)(\overline{BC})\overline{C}} \\
 &= \overline{(\overline{ABC} + \overline{BC})\overline{C}} = \overline{\overline{ABC} + \overline{BC}} = \overline{\overline{BC}(A+1)} = \overline{\overline{BC}} = BC
 \end{aligned}$$


See Figure 5-10.

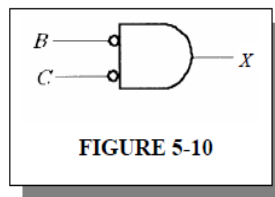


The output is dependent only on B and C . The value of A does not matter. The NOR gate behaves as a negative-AND.

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

20. See Figure 5-20.

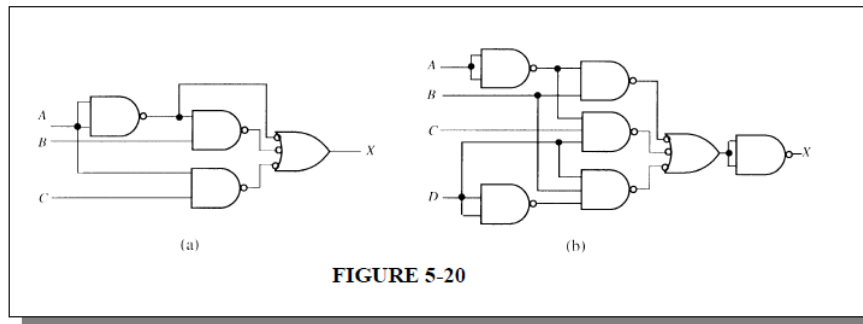


22. See Figure 5-22.

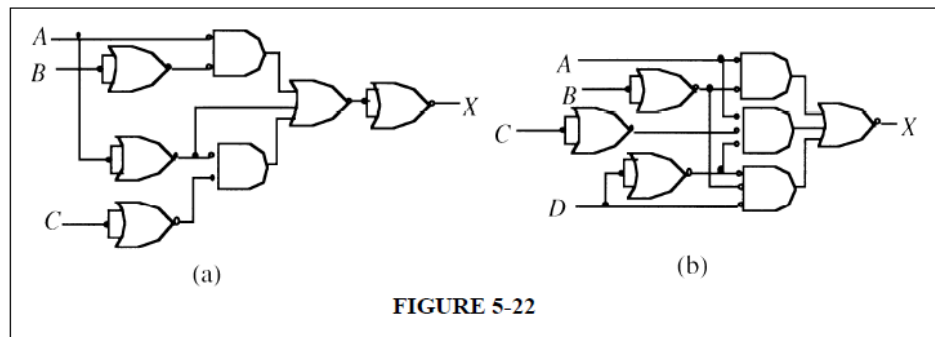

26.

$$(g) \quad X = A(CD + B) = ACD + AB$$

See Figure 5-44.

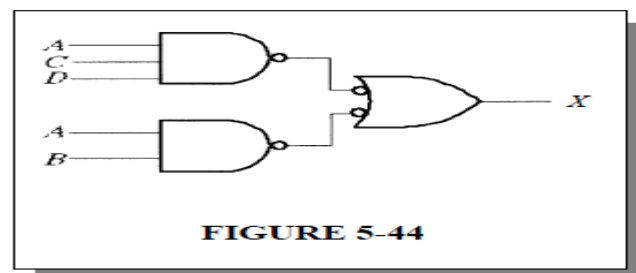

28. $X = \overline{\overline{A + B} + B} = AB\overline{B} = 0$
The output X is always LOW.